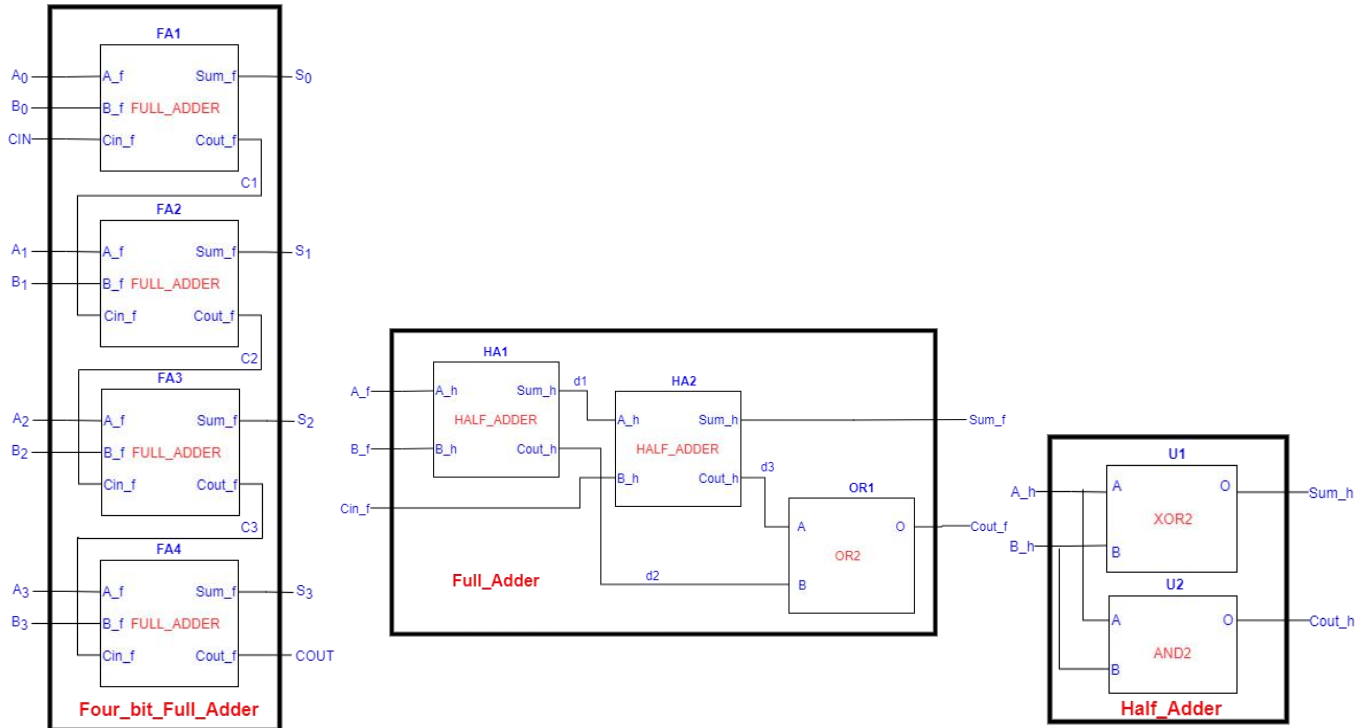


1. Structure



2. VHDL code

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity Four_bit_Full_Adder is
    Port ( A0,A1,A2,A3,B0,B1,B2,B3,CIN : in std_logic;
           S0,S1,S2,S3,COUT : out std_logic);
end Four_bit_Full_Adder;
architecture STRUCTURE of Four_bit_Full_Adder is
    component FULL_ADDER is
        port (A_f, B_f, Cin_f : in std_logic; Sum_f, Cout_f : out std_logic);
    end component FULL_ADDER;
    signal c1, c2, c3 : std_logic;
begin
    FA1: FULL_ADDER port map (A_f=>A0, B_f=>B0, Cin_f=>CIN, Sum_f=>S0, Cout_f=>C1);
    FA2: FULL_ADDER port map (A_f=>A1, B_f=>B1, Cin_f=>C1, Sum_f=>S1, Cout_f=>C2);
    FA3: FULL_ADDER port map (A_f=>A2, B_f=>B2, Cin_f=>C2, Sum_f=>S2, Cout_f=>C3);
    FA4: FULL_ADDER port map (A_f=>A3, B_f=>B3, Cin_f=>C3, Sum_f=>S3, Cout_f=>COUT);
end STRUCTURE;

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity Full_Adder is
    port (A_f, B_f, Cin_f : in std_logic;
          Sum_f, Cout_f : out std_logic);
end entity Full_Adder;
architecture STRUCTURE of Full_Adder is
    component HALF_ADDER is
        port (A_h, B_h : in std_logic;
              Sum_h, Cout_h : out std_logic);
    end component HALF_ADDER;
    component OR2 is
        port (A, B : in std_logic; O : out std_logic);
    end component OR2;
    signal d1, d2, d3 : std_logic;
begin
    HA1: HALF_ADDER port map (A_h=>A_f, B_h=>B_f, Sum_h=>d1, Cout_h=>d2);
    HA2: HALF_ADDER port map (A_h=>d1, B_h=>Cin_f, Sum_h=>Sum_f, Cout_h=>d3);
    OR1: OR2 port map (A=>d3, B=>d2, O=>Cout_f);
end STRUCTURE;

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity Half_Adder is
    port (A_h, B_h : in std_logic;
          Sum_h, Cout_h : out std_logic);
end entity Half_Adder;
architecture STRUCTURE of Half_Adder is
    component XOR2 is
        port (A, B : in std_logic; O : out std_logic);
    end component XOR2;
    component AND2 is
        port (A, B : in std_logic; O : out std_logic);
    end component AND2;
begin
    U1: XOR2 port map (A=>A_h, B=>B_h, O=>Sum_h);
    U2: AND2 port map (A=>A_h, B=>B_h, O=>Cout_h);
end STRUCTURE;

```

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity OR2 is
    port (A, B : in std_logic; O : out
          std_logic);
end entity OR2;
architecture BHV of OR2 is
begin
    O <= A or B; -- after 10 ns;
end BHV;

```

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity AND2 is
    port (A, B : in std_logic; O : out
          std_logic);
end entity AND2;
architecture dataflow of AND2 is
begin
    O <= A and B;
end dataflow;

```

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity XOR2 is
    port (A, B : in std_logic; O : out
          std_logic);
end entity XOR2;
architecture BHV of XOR2 is
begin
    O <= A xor B; --after 10 ns;
end BHV;

```

In the VHDL code we **set no delay(using delta delay) for the gate to simplify our simulation. We can easily verify the result for there is no obvious delay in waveform.** Further we will add the gate delay and see the result again.

3. Testbench code

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use ieee.numeric_std.all;


entity Four_bit_Full_Adder_tb is
-- Port ();
end Four_bit_Full_Adder_tb;
architecture Behavioral of Four_bit_Full_Adder_tb is
    COMPONENT four_bit_full_adder
    PORT(A0,A1,A2,A3,B0,B1,B2,B3,CIN: in std_logic;
         S0,S1,S2,S3,COOUT: out std_logic);
    END COMPONENT;
    signal A0_tb,A1_tb,A2_tb,A3_tb,B0_tb,B1_tb,B2_tb,B3_tb,CIN_tb: std_logic;
    signal S0_tb,S1_tb,S2_tb,S3_tb,COOUT_tb: std_logic;
begin
    uut: four_bit_full_adder PORT MAP ( A0=>A0_tb,A1=>A1_tb,A2=>A2_tb,A3=>A3_tb,
                                         B0=>B0_tb,B1=>B1_tb,B2=>B2_tb,B3=>B3_tb,CIN=>CIN_tb,
                                         S0=>S0_tb,S1=>S1_tb,S2=>S2_tb,S3=>S3_tb,COOUT=>COOUT_tb);

tb: process is
    constant PERIOD: time := 20 ns;
    constant n : integer := 9;
    variable i : integer;
begin
    for i in 0 to 2**n - 1 loop
        (A0_tb,A1_tb,A2_tb,A3_tb,B0_tb,B1_tb,B2_tb,B3_tb,CIN_tb) <= to_unsigned(i, n);
        wait for PERIOD;
    end loop;
    wait;
end process;

end Behavioral;
```

4. Simulation result

Behavior result:

 


Behavior simulation

The result is correct, **for the logic expression for the output of 4-bit full-adder is complex to write out, we do not write the 'assert' and 'report' in testbench.** We can choose several output to verify, for example:




 A:1110 B:1001 Cin:1
 Output Sum:1000 Cout:1 which is correct
 Also, another verify:




A:1001 B:1011 Cin:0
 Output Sum:0100 Cout:1 which is also correct


Post-synthesis functional simulation:

 


Post-synthesis timing simulation:

 


 Post-Implementation functional simulation:



Post-Implementation timing simulation:

 

 

Further discussion: add the delay of the gate

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity OR2 is
port (A, B: in std_logic; O: out std_logic );
end entity OR2;
architecture BHV of OR2 is
begin
    O <= A or B after 10 ns;
end BHV;
```

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity AND2 is
port (A, B: in std_logic; O: out std_logic );
end entity AND2;
architecture dataflow of AND2 is
begin
    O <= A and B;
end dataflow;
```

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity XOR2 is
port (A, B: in std_logic; O: out std_logic );
end entity XOR2;
architecture BHV of XOR2 is
begin
    O <= A xor B after 10 ns;
end BHV;
```

Behavior simulation result:

